 


Non-switching Class AB design

The schematic below partly shows the design by Jager et al. [1] to realize a non-switching class AB output stage. The control current from the input stage is called I_{in} . The output (OUT) is taken from the Darlington output transistors Q4/Q6 and Q5/Q7. The power transistors are Q6 and Q7, while the drivers are Q4 and Q5. Please notice that these transistors operate in common emitter configuration. This implies that the open loop output impedance is quite high, demanding a fair amount of open loop gain to realize a closed loop low output impedance. The control loop is realized by the transistors Q₁-Q₄.



It is seen that:

$$V_{BIAS} = V_{BE1} + V_{BE2} = V_{BE3} + V_{BE4} \quad (1)$$

In general we have (Ebers-Moll, approximately):

$$I_C = I_S e^{V_{BE}/V_T} \quad (2)$$

Where:

I_C : Collector current

V_{BE} : Base-emitter voltage

I_S : Leakage current

V_T : Thermal voltage, $V_T = kT/e$

k : Boltzmann constant: $1.3806 \cdot 10^{-23}$ J/K

T : Absolute temperature [K]

e : Elementary charge: $1.602 \cdot 10^{-19}$ C

From eq. 2, we then have:

$$V_{BE} = V_T \ln \frac{I_C}{I_S} \quad (3)$$

From eq.1 and 3, we can then exploit:

$$V_{BIAS} = V_T \ln \frac{I_{C1}}{I_S} + V_T \ln \frac{I_{C2}}{I_S} = V_T \ln \frac{I_{C3}}{I_S} + V_T \ln \frac{I_{C4}}{I_S} \quad (4)$$

Since approximately $I_{C1} = I_{C2} = I_{Ref}$, this leads to:

$$V_{BIAS} = V_T \ln \frac{I_{Ref}^2}{I_S^2} = V_T \ln \frac{I_{C3} \cdot I_{C4}}{I_S^2} \quad (5)$$

Which leads to the expression:

$$I_{Ref}^2 = I_{C3} \cdot I_{C4} \quad (6)$$

We can assume that:

$$I_{C4} = I_{C5} = h_{FE} I_{C3} \quad (7)$$

Where h_{FE} is the transistor current gain, assumed the same for all the transistors. Combining eq. 6 and 7, then gives:

$$I_{C4}^2 = h_{FE} \cdot I_{Ref}^2 \Rightarrow I_{C4} = I_{C5} = I_{Ref} \sqrt{h_{FE}} \quad (8)$$

It is seen that the function of Q_1 is to isolate Q_6 from the control loop, thus avoiding thermal runaway and switching distortion.

The current gain I_{OUT}/I_{In} for the output stage is approximately given by:


$$A_1 = h_{FE}^2 \quad (9)$$

The control loop can be optimised by adding another transistor Q_0 as shown in the figure below. Now the collector current of Q_1 is reduced with the current gain h_{FE} . So inserting $I_{Ref} = I_{C2} = h_{FE} I_{C1}$ into eq. 4, we have:

$$V_{BIAS} = V_T \ln \frac{I_{Ref}}{h_{FE} \cdot I_S} + V_T \ln \frac{I_{Ref}}{I_S} = V_T \ln \frac{I_{C3}}{I_S} + V_T \ln \frac{I_{C4}}{I_S} \quad (10)$$

This leads to:
 
$$\frac{I_{Ref}^2}{h_{FE}} = I_{C3} \cdot I_{C4} \quad (11)$$



Using eq. 7, we can write:

$$\frac{I_{\text{Ref}}^2}{h_{\text{FE}}} = I_{\text{C3}} \cdot I_{\text{C4}} = \frac{I_{\text{C4}}}{h_{\text{FE}}} \cdot I_{\text{C4}} \quad (12)$$

Then we have the expression (compare to eq. 8):

$$I_{\text{C4}} = I_{\text{C5}} = I_{\text{Ref}} \quad (13)$$

As a result the bias current of the power transistors now is given by:

$$I_{\text{C6}} = I_{\text{C7}} = h_{\text{FE}} \cdot I_{\text{Ref}} \quad (14)$$

The control loop now controls the bias current of the driver transistors directly with the means of the reference current I_{Ref}.

Reference:

1. Wim de Jager, Erik van der Ven and Ed van Tuyt: A new Class-AB design, Electronics World December 1999.

© Knut Harald Nygaard